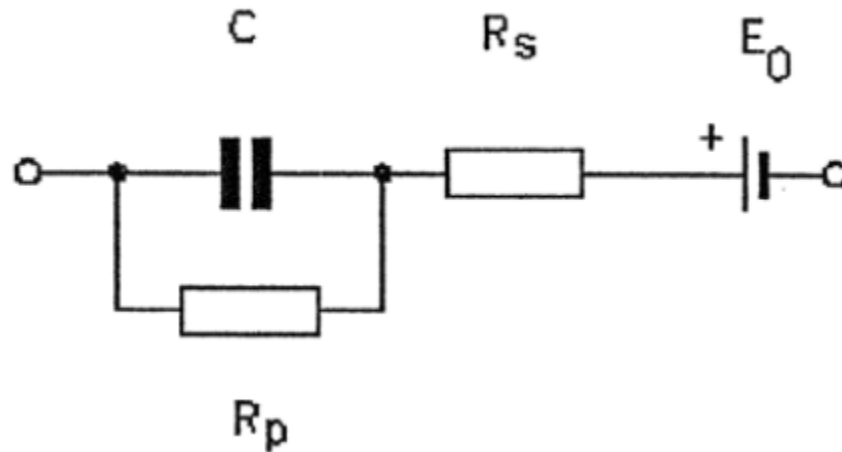


1.



C : The capacitance across the electrode-electrolyte and the surface layer (example muscle/skin).

This capacitance can store charges and could interfere with certain range of signals

R_p : Polarized resistance, is the resistance between the electrode-electrolyte and the surface of the interested biopotential source.

R_s : Series Resistance associated with electrolyte or sometimes electrode.

E_0 : Half-cell potential, is in essence the voltage difference between the electrode and its reference when no current flows through.

2. By using needle or wire for an invasive electrode we can expect the following:



For Capacitance, we can see a decrease in capacitance due to lower surface area of the electrode and a smaller distance between electrode and muscle/nerve, which could lead to lower noise

For R_p we can also expect the resistance to be much lower since a lot of layers of skin and other tissues no longer interfere with the signal path. Which should have an increase in Signal to Noise Ratio.

E_0 may change since electrode potential may now be different, but assuming that electrolyte concentration remains the same there's probably not a lot of difference. Physiological response to a puncture/wound may have some time dependent changes that might affect the Half cell potential by small amounts.

Series potential probably doesn't change a lot.

3.

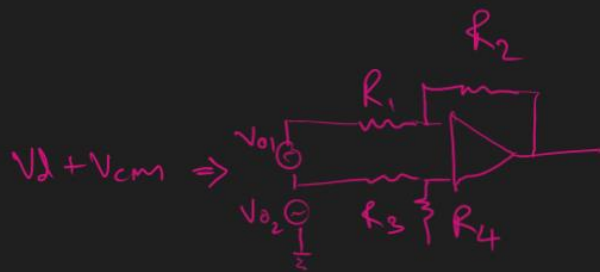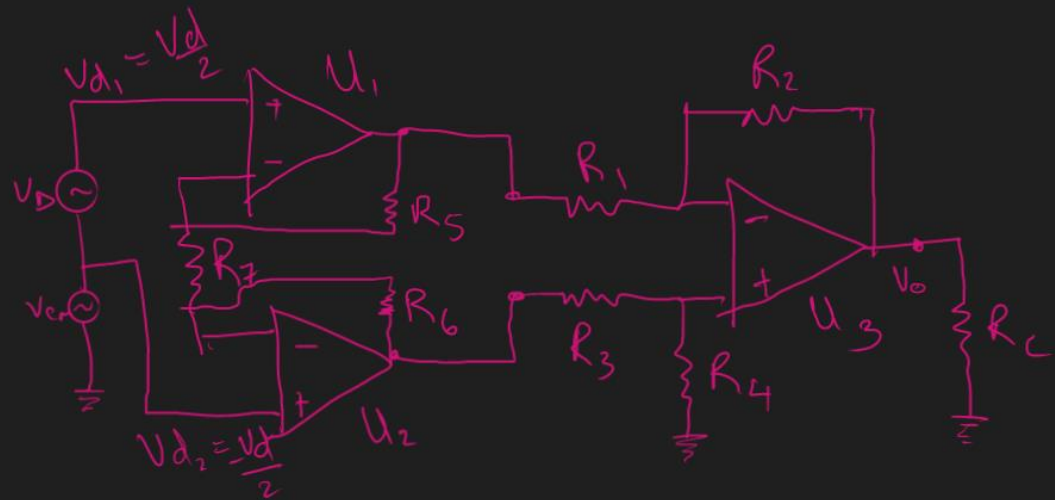

⇒ We can solve A_D independently for Stage 1 & Stage 2 ; then we $A_{D1} \times A_{D2} = A_D$ for the whole system

Stage 1

$$V_D = V_{D1} - V_{D2}$$

$$V_{O1} - V_{O2} = \left(\frac{V_{D1} - V_{D2}}{R_7} \right) (R_5 + R_6 + R_7)$$

$$A_{V1} = \frac{V_{O1} - V_{O2}}{V_D} = \frac{\frac{V_D}{2} - \left(-\frac{V_D}{2} \right)}{R_7 V_D} (R_5 + R_6 + R_7)$$

$$A_{V1} = 1 + \frac{R_5 + R_6}{R_7}$$

Stage 2

$$V_O = -\frac{R_2}{R_1} V_{D1} + \left(\frac{R_4}{R_3 + R_4} \right) \left(\frac{R_1 + R_2}{R_1} \right) - \frac{V_D}{2}$$

$$A_{V2} = \frac{V_{O2}}{V_D} = -\frac{R_2}{2R_1} - \frac{R_4(R_1 + R_2)}{2R_1(R_3 + R_4)}$$

$$A_V = A_{V1} \times A_{V2} = \left(1 + \frac{R_5 + R_6}{R_7} \right) \left(-\frac{R_2}{2R_1} - \frac{R_4(R_1 + R_2)}{2R_1(R_3 + R_4)} \right)$$

$$\begin{aligned}
 A_V &= A_{V_1} \times A_{V_2} = \left(1 + \frac{R_5 + R_6}{R_7}\right) \left(-\frac{R_2}{2R_1} - \frac{R_4(R_1 + R_2)}{2R_1(R_3 + R_4)}\right) \\
 &= \left(1 + \frac{R_5 + R_6}{R_7}\right) \left(\frac{+R_2R_3 + R_2R_4 + R_4R_1 + R_2R_4}{2R_1R_3 + 2R_1R_4}\right) \\
 &= \left(\frac{R_7 + R_5 + R_6}{R_7}\right) \left(\frac{+R_2R_3 + R_2R_4 + R_4R_1 + R_2R_4}{2R_1R_3 + 2R_1R_4}\right) \\
 &= \left(1 + \frac{R_5 + R_6}{R_7}\right) \left(\frac{1}{2} \frac{R_2R_3 + 2R_2R_4 + R_4R_1}{R_1(R_3 + R_4)}\right) \\
 \boxed{A_D} &= \frac{1}{2} \frac{R_2R_3 + 2R_2R_4 + R_4R_1}{R_1(R_3 + R_4)} + \frac{1}{2} \frac{(R_5 + R_6)(R_2R_3 + 2R_2R_4 + R_4R_1)}{R_7R_1(R_3 + R_4)}
 \end{aligned}$$

4.

Using Similar Reasoning

$$\text{for } A_{CM} = A_{CM_1} \times A_{CM_2}$$

$$\&\text{ then } CMMR = \frac{A_D}{A_{CM}} = \frac{A_{D_1} \times A_{D_2}}{A_{CM_1} \times A_{CM_2}}$$

\rightarrow for A_{cm} $V_d = 0$ & $V^+ = V^- = V_{cm}$

$\Rightarrow \frac{V_{ocm1}}{V_{cm1}} = \frac{V_c - V_c}{R_7} (R_5 + R_6 + R_7)$

$\frac{0}{V_c} = ??$

technically since they are unity gain buffers ($I_7 = 0$ since R_7 has a potential of 0 due to virtual ground)

$\Rightarrow A_{cm1} = \underline{1}$

$\frac{V_{ocm2}}{V_{cm2}} = \frac{-R_2}{R_1} V_c + \left(\frac{R_4}{R_3 + R_4} \right) \left(\frac{R_1 + R_2}{R_1} \right) V_c$

$= -\frac{R_2}{R_1} + \frac{R_4(R_1 + R_2)}{R_1(R_3 + R_4)}$

$= \frac{-R_2(R_3 + R_4) + R_4R_1 + R_4R_2}{R_1(R_3 + R_4)}$

$= \frac{-R_2R_3 - R_2R_4 + R_4R_1 + R_4R_2}{R_1(R_3 + R_4)}$

$= \frac{R_4R_1 - R_2R_3}{R_1(R_3 + R_4)}$

$\Rightarrow A_{cm} = 1 \times A_{cm2}$

$= \frac{R_4R_1 - R_2R_3}{R_1(R_3 + R_4)}$


$\Rightarrow CMMR = \frac{\frac{\frac{1}{2} R_2 R_3 + \frac{1}{2} R_2 R_4 + \frac{1}{2} R_4 R_1 + \frac{1}{2} R_4 R_2}{R_1(R_3 + R_4)} + \frac{1}{2} (R_5 + R_6) \left(\frac{R_2 R_3 + R_2 R_4 + R_4 R_1 + R_4 R_2}{R_7 R_1(R_3 + R_4)} \right)}{\frac{R_4R_1 - R_2R_3}{R_1(R_3 + R_4)}}$

$= \frac{1}{2} \cancel{R_2R_3 + R_2R_4 + R_4R_1 + R_4R_2}$

I didn't want to simplify and my sketching tablet keeps disconnecting

- Due to additional Resistance and capacitance the CMMR would be lower and would be affected by the frequency as well depending on both R_g and C

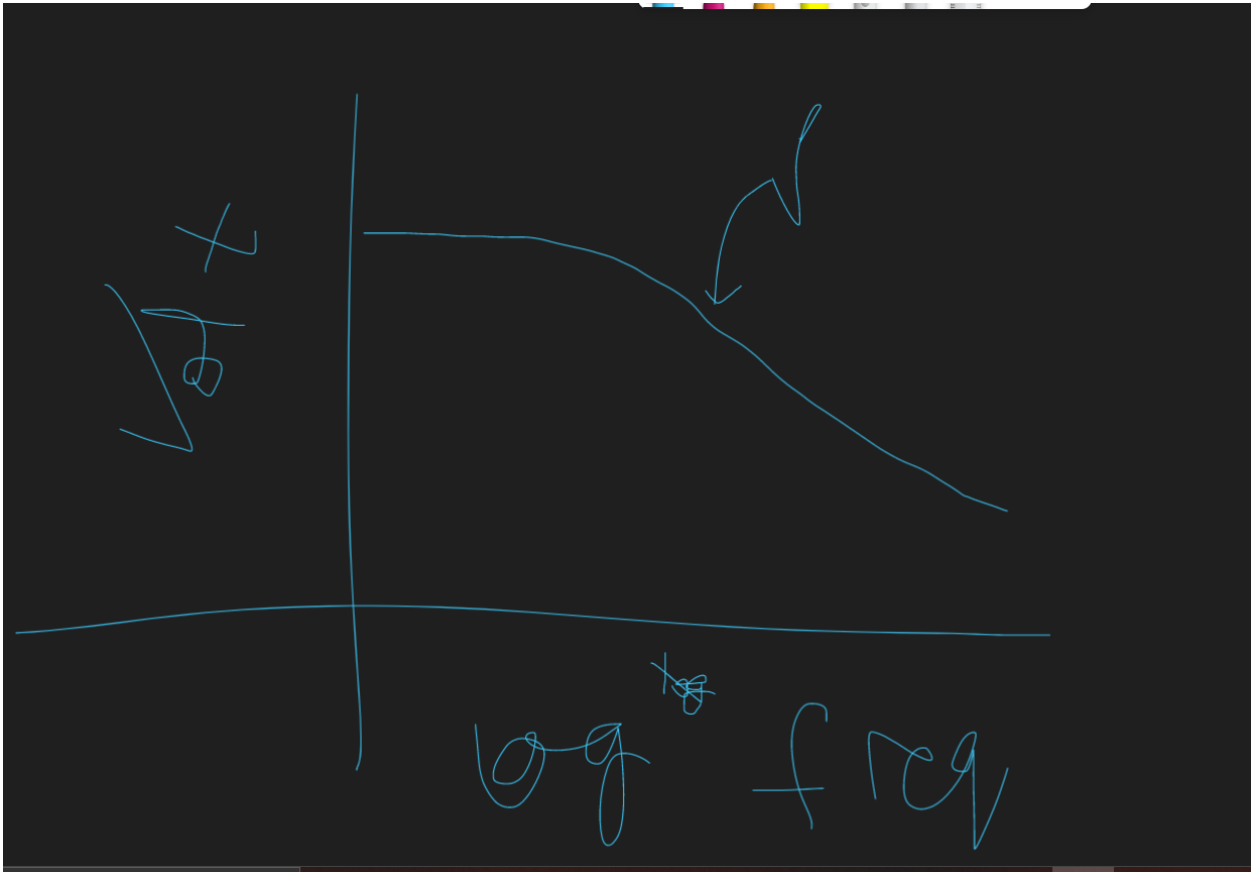Not sure how this would behave and cannot sketch




slope would be a function of rg and C

6. q7 is on next page.

7.

a.

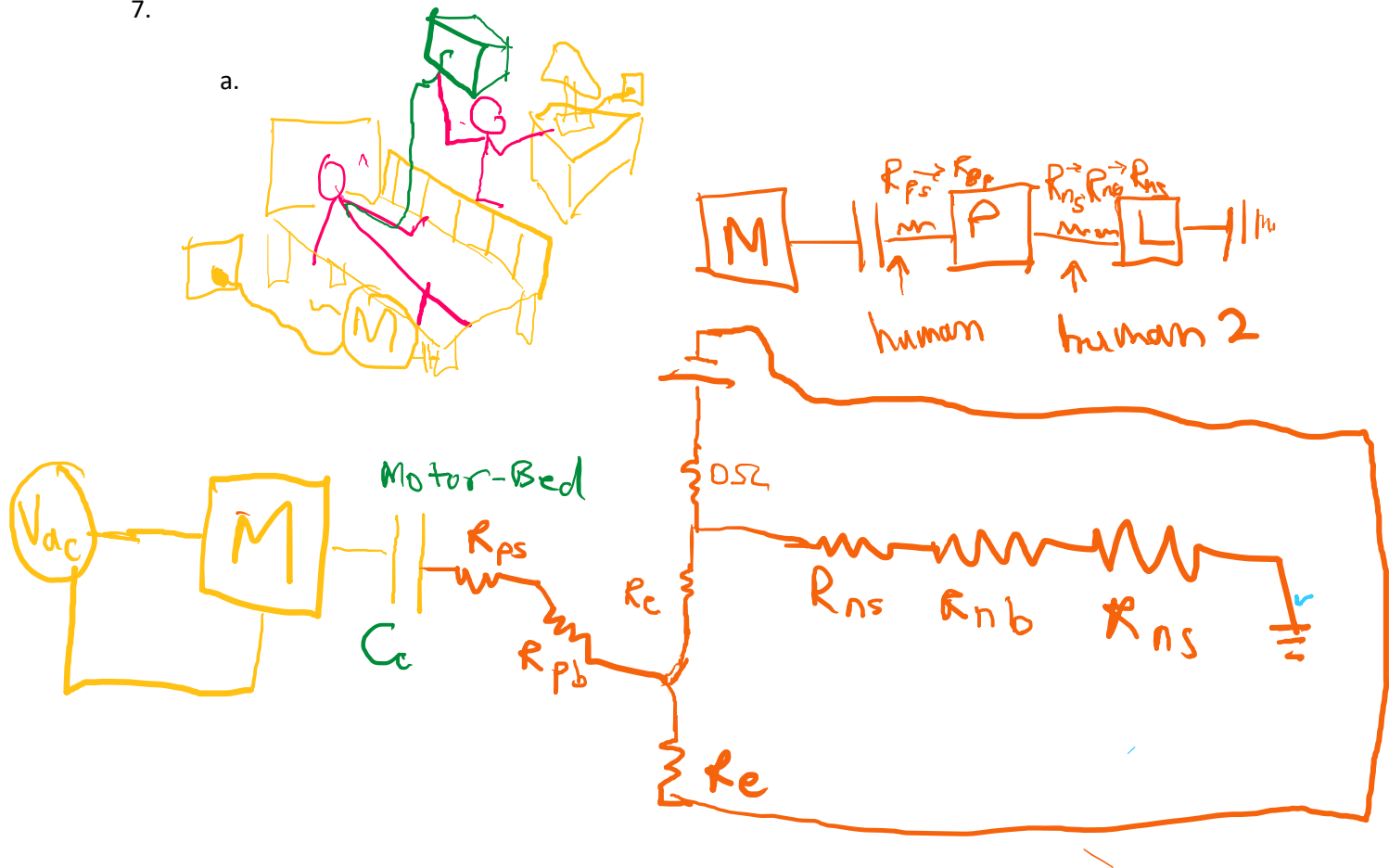

- b. For the case of nurse, we know that the motor-bed is higher potential since it's not grounded. The parasitic capacitance would allow the 60hz 120V to flow through.

In this case it would flow through the patient skin → patient body → Catheter → electrode lead → nurse skin → nurse body → nurse skin → ground (lamp)

$$I_{\text{nurse}} = \frac{V_{\text{rms}}}{Z}$$

$$Z = R_{\text{total}} + \frac{1}{j\omega C_c}$$

$$R_{\text{total}} = R_{ps} + R_{pb} + R_e + R_{ns} + R_{nb} + R_{ns}$$

$$I_{nurse} = \frac{120}{\frac{1}{2\pi 60(2500 \cdot 10^{-12})} + 3 \cdot 100 \cdot 10^3 + 2 \cdot 500 + 1000} = 88.04 \mu\text{A}$$

The current is too small for any perception for macro shocks,

- c. In the case of the patient they would get a micro-shock and since this is above the $10\mu\text{A}$ and also above $60\mu\text{A}$ threshold, the patient can have fibrillation